# A touch controlled throttle for electric bicycles.

The first part of this document presents the electronic circuit of a touch throttle for use with electric motor controllers. The second part presents a design example based on the circuit. The example circuit is compatible with many electric bicycle (e-bike) motor controllers.

## Part I

#### A touch throttle for motor control

Many electric personal transportation vehicles such as e-bikes, electric scooters, and others are equipped with motor controllers that include some form of throttle. Many controllers adjust the power applied to the motor depending on a voltage signal from the throttle. The controller provides power to the throttle by means of supply voltage and ground lines and the throttle provides a voltage signal to the controller referenced to the ground line. The touch operated throttle is an alternative to available throttles which are operated by motion of the wrist (full and half twist throttles) or finger (thumb and trigger throttles).

The <u>Spectra Symbol</u> company produces a family of <u>linear position sensors</u> that include force sensitive variable resistors. The resistance of these devices changes when force is applied, for example, by touching with a finger. The throttle design in this document is based on the <u>ThinPot</u> device. A general schematic for the throttle is shown in **figure 1**.



**Vs** and **GND** are the power lines provided by the controller to the throttle. **Signal** is the voltage provided by the throttle to the controller, referenced to the ground line.

**Rv** is the variable resistor(ThinPot).

**Q** and **Re** are configured as a common collector amplifier or emitter follower. These should be included if the input resistance of the controller is small. The variable terminal of Rv can be connected directly to controllers that have a large input resistance with a response that will be close to linear. However, for controllers with input resistance close to or below the resistance of Rv the linearity will be poor. The high input resistance of the emitter follower will eliminate this problem and its output can drive both low and high input resistance controllers. Transistor Q can be any npn bipolar junction transistor (BJT) with maximum voltage ratings greater than Vs. The schematic shown is for positive Vs, for negative Vs a pnp BJT is used.

figure 1

**Rsh** and **Rsl** are series resistors that set the voltage range across Rv. Most controllers do not respond to the full voltage range of 0 to Vs, instead responding from a minimum value (Vmin) to a maximum value (Vmax). Rsl and Rsh determine the Vmin and Vmax values respectively that are presented to the controller. If Rsl an Rsh are not needed in an application, at least one of them should be included as a current limiting resistor. Otherwise, if both ends of Rv are touched at the same time it will result in a short that will destroy the conductive traces of Rv. If the circuit requires the use of the emitter follower, the value of Vmin and Vmax should be adjusted to account for the base to emitter voltage drop of the tansistor.

**Rpd** is a pull down resistor. The variable terminal of the ThinPot floats when not pressed, Rpd is needed to provide a "return to zero" function when the throttle is released. The linearity of the output of Rv is affected by Rpd, its value should be large compared to Rv to minimize this effect. Some e-bike displays expect a non-zero value when the throttle is released. To satisfy this requirement Rpd is connected to the Rv-Rsl node. If the controller or display do not have the requirement, Rpd can be connected to ground.

**Sw** is a single pole single throw normally open momentary action switch. Sw is a safety cutoff switch that should be included when testing a design. Operation of the throttle requires that Sw be pressed. Releasing Sw, as in case of an accident, will drive the signal to zero.

### Part II

#### A touch throttle circuit design example

Most e-bike controllers use a "standard" 3 line throttle connection that provides +5 volts and ground(0V) lines for power, and a signal input line. The values for Vmin and Vmax vary between controller brands but most are compatible with throttles based on linear hall effect sensors that have approximate Vmin and Vmax values of 0.8V and 4.2V respectively. The circuit in this example will be used with a controller that provides 5 volts to the throttle and responds to voltages between 1.1 and 4.2 volts. We want Vmin slightly below 1.1V and Vmax slightly above 4.2V.

The circuit schematic for the touch throttle is shown in **figure 2**.



All fixed resistors are 1/4 watt, 5% tolerance. **Rv (10Kohms)** is the variable resistor (ThinPot). **Rpd (100Kohms)** is the pull down resistor.

**Rsl(4.7Kohms)** is used to set Vmin to about 1.6 volts. We selected this value to offset the base to emitter voltage drop of about 0.7 volts of the transistor. This value is the closest E12 standard resistor value to get Vmin, the next E12 value of 5.6Kohms results in Vmin too close to 1.1V. The resulting value of Vmin at the emitter of Q1 will be about 0.9 volts. For Vmax the value is about 4.3 volts so Rsh is not required. **Q** is a BC547B npn bipolar junction transistor.

**Re(4.7Kohms)** was selected to limit the number of different components. The no load current required by the throttle will be below 2 milliamperes.

We have tested the above circuit with several e-bikes. A mid motor integrated controller and color display, a throttle only 500 Watt brushed motor controller without a display, and a 1500 Watt controller used with a brushless hub motor and a monochrome LCD display. In all tests the e-bikes performed in a normal fashion.